Case study 3: Circuits as Resonators, Sensors, and Filters

ESE 105

Name: FILL IN HERE

function myFilterCircuit(Vin,h) receives a time-series voltage sequence sampled with interval h, and returns the output voltage sequence produced by a circuit

inputs: Vin - time-series vector representing the voltage input to a circuit h - scalar representing the sampling interval of the time series in seconds

outputs: Vout - time-series vector representing the output voltage of a circuit

```
%C_3 is the lowest note in this part of the hallelujah chorus - that's
%about 130 Hz. D 5 is the highest note, that's about 590 Hz. I'm going
%filter everything out that's in between
function Vout = myFilterCircuit(Vin,h)
R = 4450000/(1711*pi);
L = 5000/(1711*pi^2);
C = 10^{-6};
VC = 0;
V_data = [1, length(Vin)];
I = 0;
for k=1:length(Vin)
    A = [1, h/C; -h/L, 1-h*R/L];
    x_k = [V_C, I]';
    B = [0, h/L]';
    x k f = A*x k + B*Vin(k, 1);
    V_{data}(1, k) = I*R;
    V C = x k f(1, 1);
    I = x_k_f(2, 1);
end
Vout = V data';
end
Not enough input arguments.
Error in myFilterCircuit (line 27)
V_data = [1, length(Vin)];
```

Published with MATLAB® R2021a